

# Communicating State Machines

Martin Schoeberl

Technical University of Denmark  
Embedded Systems Engineering

April 8, 2021

# Overview

- ▶ Repeat functions and parameters
- ▶ Input processing
- ▶ Ready/valid interface
- ▶ A little bit of Scala
- ▶ Hardware generators

# Last (and Today's) Lab

- ▶ Display multiplexer
  - ▶ Input are 16 switches for 4 hexadecimal digits
- ▶ Almost 12/27 have already finished. This is GREAT!
- ▶ Please show it a TA when finished for a “tick”
- ▶ There is a simulation available, show it
- ▶ Maybe extend it with binary to BCD conversion
  - ▶ This is optional/advanced material
- ▶ You can also start to work on the full Vending Machine
  - ▶ Top-level, pin definition, and a simple tester are in:
  - ▶ <https://github.com/schoeberl/chisel-lab/tree/master/vending>

# Next Labs

- ▶ Next week:
  - ▶ Almost 4 hours lab
  - ▶ Just vending machine specification recap
  - ▶ Maybe questions
- ▶ Work on the full Vending Machine

# Functions

- ▶ Circuits can be encapsulated in functions
- ▶ Each *function call* generates hardware
- ▶ A function is defined with `def name`
- ▶ Similar to a method in Java
- ▶ Simple functions can be a single line

```
def adder(v1: UInt, v2: UInt) = v1 + v2
```

```
val add1 = adder(a, b)
```

```
val add2 = adder(c, d)
```

# More Function Examples

- Functions can also contain registers

```
def addSub(add: Bool, a: UInt, b: UInt) =  
  Mux(add, a + b, a - b)
```

```
val res = addSub(cond, a, b)
```

```
def rising(d: Bool) = d && !RegNext(d)
```

```
val edge = rising(cond)
```

# The Counter as a Function

- ▶ Longer functions in curly brackets
- ▶ Last value is the return value

```
def counter(n: UInt) = {  
  
    val cntReg = RegInit(0.U(8.W))  
  
    cntReg := cntReg + 1.U  
    when(cntReg == n) {  
        cntReg := 0.U  
    }  
    cntReg  
}  
  
val counter100 = counter(100.U)
```

# Functional Abstraction

- ▶ Functions for repeated pieces of logic
- ▶ May contain state
- ▶ Functions may return *hardware*
- ▶ More lightweight than a Module



# Parameterization

```
class ParamChannel(n: Int) extends Bundle {  
  val data = Input(UInt(n.W))  
  val ready = Output(Bool())  
  val valid = Input(Bool())  
}
```

```
val ch32 = new ParamChannel(32)
```

- ▶ Bundles and modules can be parametrized
- ▶ Pass a parameter in the constructor

## A Module with a Parameter

```
class ParamAdder(n: Int) extends Module {  
  val io = IO(new Bundle{  
    val a = Input(UInt(n.W))  
    val b = Input(UInt(n.W))  
    val c = Output(UInt(n.W))  
  })  
  
  io.c := io.a + io.b  
}
```

- Parameter can also be a Chisel type

# Use the Parameter


```
val add8 = Module(new ParamAdder(8))  
val add16 = Module(new ParamAdder(16))
```

- ▶ Can be used for the display multiplexing configuration
- ▶ Switching between a constant for simulation and a constant for the FPGA

# Input Processing

- ▶ Input signals are not synchronous to the clock
- ▶ May violate setup and hold time of a flip-flop
- ▶ Can lead to metastability
- ▶ Signals need to be *synchronized*
- ▶ Using two flip-flops
- ▶ Metastability cannot be avoided
- ▶ Assumption is:
  - ▶ First flip-flop may become metastable
  - ▶ But will resolve within the clock period

# Input Synchronizer

 


```
val btnSync = RegNext(RegNext(btn))
```

# Bouncing Buttons

- ▶ Buttons and switches need some time to transition between on and off
- ▶ May bounce between the two values
- ▶ Without processing we detect more than one event
- ▶ Solution is to filter out bouncing
  - ▶ Can be done electrically (R + C + Schmitt trigger)
  - ▶ That is why you have the extra PCB with the buttons
  - ▶ But we can also do this digitally
- ▶ Assume bouncing time  $t_{bounce}$
- ▶ Sample at a period  $T > t_{bounce}$
- ▶ Only use sampled signal

# Sampling for Debouncing

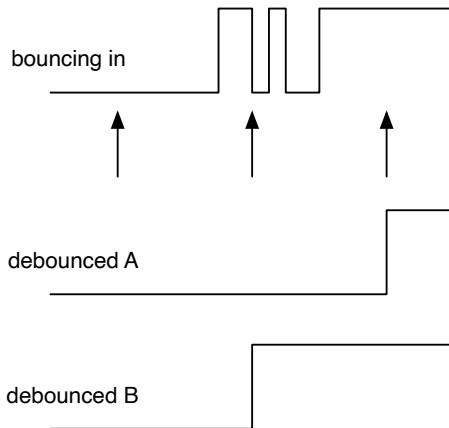

# Sampling for Debouncing

```
val FAC = 1000000000/100
```

```
val btnDebReg = Reg(Bool())
```

```
val cntReg = RegInit(0.U(32.W))
```

```
val tick = cntReg == (FAC-1).U
```

```
cntReg := cntReg + 1.U
```

```
when (tick) {
```

```
    cntReg := 0.U
```

```
    btnDebReg := btnSync
```

```
}
```


- ▶ We already know how to do this!
- ▶ Just generate timing with a counter
- ▶ We sample at 100 Hz (bouncing below 10 ms)



# Noisy Input Signal

- ▶ Sometimes input may be noisy
- ▶ May contain spikes
- ▶ Filtering with majority voting
- ▶ Majority voting of the sampled input signal
- ▶ However, this is seldom needed
- ▶ Not for the buttons

# Majority Voting

 

# Majority Voting

```
val shiftReg = RegInit(0.U(3.W))
when (tick) {
    // shift left and input in LSB
    shiftReg := Cat(shiftReg(1, 0), btnDebReg)
}
// Majority voting
val btnClean = (shiftReg(2) & shiftReg(1)) |
    (shiftReg(2) & shiftReg(0)) | (shiftReg(1) &
    shiftReg(0))
```

# Detecting the Press Event

- ▶ Edge detection
- ▶ You have seen this before
- ▶ Just to complete the input processing

```
val risingEdge = btnClean & !RegNext(btnClean)

// Use the rising edge of the debounced and
// filtered button to count up
val reg = RegInit(0.U(8.W))
when (risingEdge) {
    reg := reg + 1.U
}
```

# Combine Input Processing with Functions

- ▶ Using small functions to abstract the processing
- ▶ [Debounce.scala](#)


# Communicating State Machines

- ▶ We did refactor a large FSM into smaller ones last week
- ▶ FSMs *communicate*
- ▶ Simple communication is your input processing to FSM with datapath
- ▶ More complex FSMs may exchange data with handshaking

# Handshaking

- ▶ Producer of data and consumer need to agree when data is transferred
- ▶ Producer tells when data is available/valid with a valid signal
- ▶ Consumer tells when it is ready to receive data with a ready signal
- ▶ When both are asserted the transfer takes place
- ▶ Also called *flow control*


# Ready-Valid Interface

 


- Ready-valid flow control




# Ready-Valid Interface, Early Ready

 

# Ready-Valid Interface, Late Ready

 

# Single Cycle and Back-to-Back

 

# Common Interface

- So common interface that Chisel defines a DecoupledIO

```
class DecoupledIO[T <: Data](gen: T) extends
  Bundle {
    val ready = Input(Bool())
    val valid = Output(Bool())
    val bits  = Output(gen)
  }
```

# First Summary and Break

- ▶ Main topic of today done
- ▶ Following is advanced material
- ▶ A little bit of Scala
- ▶ How to write hardware generators
- ▶ Maybe extend your display to show decimal number
- ▶ But first 10 minutes BREAK

# Binary-Coded Decimal (BCD)

- ▶ Your current display shows numbers in hexadecimal
  - ▶  $15_{10}$  is displayed as  $0F_{16}$
  - ▶ Which is in binary: 00001111
  - ▶ We would like to see it as a '1' followed by a '5'
  - ▶ Which is in binary: 0001 0101
- ▶ Convert from binary to binary-coded decimal (BCD)
  - ▶ But only for the display
  - ▶ Computing in BCD is hard

# Binary to BCD Conversion Table

```
val bincode = io.sw(7,0)
val bcd = WireDefault(bincode)

switch(bincode) {
  is(0.U) { bcd := "b0000_0000".U }
  is(1.U) { bcd := "b0000_0001".U }
  is(2.U) { bcd := "b0000_0010".U }
  // ... some more
  is(9.U) { bcd := "b0000_1001".U }
  is(10.U) { bcd := "b0001_0000".U }
  is(11.U) { bcd := "b0001_0001".U }
  is(12.U) { bcd := "b0001_0010".U }
  // ... and many more entries
}

dispMux.io.price := bcd
```

# Binary-Coded Decimal (BCD)

- ▶ Conversion is a table (= function)
- ▶ Combinational logic
- ▶ We *could* do the table manually
  - ▶ But it is large
  - ▶ The table has 100 entries to convert 0 to 99 to BCD
- ▶ Let's write a program for this
  - ▶ We could use Java, Python, TCL,...
- ▶ We will write our first *hardware generator*
- ▶ First we need a little bit of Scala



# Chisel and Scala

- ▶ Chisel is a library written in Scala
  - ▶ Import the library with `import chisel3._`
- ▶ Chisel code is Scala code
- ▶ When it is run is *generates* hardware
  - ▶ Verilog for synthesize
  - ▶ Scala netlist for simulation (testing)
- ▶ Chisel is an embedded domain specific language
- ▶ Two languages in one can be a little bit confusing

# Scala

- ▶ Is object oriented
- ▶ Is functional
- ▶ Strongly typed with very good type inference
- ▶ Runs on the Java virtual machine
- ▶ Can call Java libraries
- ▶ Consider it as Java++
  - ▶ Can almost be written like Java
  - ▶ With a more lightweight syntax

# Scala Hello World

```
object HelloScala extends App{  
  println("Hello Chisel World!")  
}
```

- ▶ Compile with `scalac` and run with `scala`
- ▶ You can even use Scala as a scripting language
- ▶ Or run with `sbt run`
- ▶ Show both

# Scala Values and Variables

- ▶ Scala has two type of variables: vals and vars
- ▶ A val cannot be reassigned, it is a constant
- ▶ We use a val to name a hardware component in Chisel

```
// A value is a constant  
val zero = 0  
// No new assignment is possible  
// The following will not compile  
zero = 3
```

- ▶ Types are usually inferred
- ▶ But can be explicitly stated as follows

```
val number: Int = 42
```

# Scala Variables

- ▶ A var can be reassigned, it is like a classic variable
- ▶ We use a var to write a hardware generator in Chisel

```
// We can change the value of a var variable  
var x = 2  
x = 3
```

# Simple Loops

```
// Loops from 0 to 9
// Automatically creates loop value i
for (i <- 0 until 10) {
  println(i)
}
```

- We use a loop to generate hardware components

# Scala for Loop for Circuit Generation

```
val shiftReg = RegInit(0.U(8.W))  
  
shiftReg(0) := inVal  
  
for (i <- 1 until 8) {  
  shiftReg(i) := shiftReg(i-1)  
}
```

- ▶ for is Scala
- ▶ This loop generates several connections
- ▶ The connections are parallel hardware
- ▶ This is a shift register

# Conditions

```
for (i <- 0 until 10) {  
  if (i%2 == 0) {  
    println(i + " is even")  
  } else {  
    println(i + " is odd")  
  }  
}
```

- ▶ Executed at runtime, when the circuit is created
- ▶ This is *not* a multiplexer



# Scala Arrays and Lists

```
// An integer array with 10 elements
val numbers = new Array[Int](10)
for (i <- 0 until numbers.length) {
  numbers(i) = i*10
}
println(numbers(9))
```

```
// List of integers
val list = List(1, 2, 3)
println(list)
// Different form of list construction
val listenum = 'a' :: 'b' :: 'c' :: Nil
println(listenum)
```

# Scala Classes

```
// A simple class
class Example {
  // A field, initialized in the constructor
  var n = 0

  // A setter method
  def set(v: Int) = {
    n = v
  }

  // Another method
  def print() = {
    println(n)
  }
}
```

# Scala (Singleton) Object

```
object Example {}
```

- ▶ For *static* fields and methods
  - ▶ Scala has no static fields or methods like Java
- ▶ Needed for `main`
- ▶ Useful for helper functions

# Singleton Object for the main

```
// A singleton object
object Example {

  // The start of a Scala program
  def main(args: Array[String]): Unit = {

    val e = new Example()
    e.print()
    e.set(42)
    e.print()
  }
}
```

- Compile and run it with sbt (or within Eclipse/IntelliJ):

```
sbt "runMain Example"
```

# Conditional Circuit Generation

```
class Base extends Module { val io = new Bundle() }  
class VariantA extends Base { }  
class VariantB extends Base { }  
  
val m = if (useA) Module(new VariantA())  
        else Module(new VariantB())
```

- ▶ if and else is Scala
- ▶ if is an expression that returns a value
  - ▶ Like “cond ? a : b;” in C and Java
- ▶ This is not a hardware multiplexer
- ▶ Decides which module to generate
- ▶ Could even read an XML file for the configuration

## A Table with a Chisel Vec

- ▶ A Chisel Vec is a collection of signals or registers
- ▶ Similar to an Array in other languages
- ▶ Vec in a Wire is a combinational table
- ▶ Vec in a Reg is a collection of registers
- ▶ Create with number of elements and hardware type

```
val v = Wire(Vec(3, UInt(4.W)))
```

# A Combinational Vec

- ▶ A combinational Vec is basically a multiplexer
- ▶ Input signal/wire connected with a constant index
- ▶ Output select with a Chisel UInt signal

```
v(0) := 1.U
```

```
v(1) := 3.U
```

```
v(2) := 5.U
```

```
val idx = 1.U(2.W)
```

```
val a = v(idx)
```

- ▶ Also convenient to represent a larger table
  - ▶ Instead of a switch table
  - ▶ Input can be *generated* with Scala code

# Binary to BCD Conversion

```
import chisel3._

class BcdTable extends Module {
  val io = IO(new Bundle {
    val address = Input(UInt(8.W))
    val data = Output(UInt(8.W))
  })

  val table = Wire(Vec(100, UInt(8.W)))

  // Convert binary to BCD
  for (i <- 0 until 100) {
    table(i) := (((i/10)<<4) + i%10).U
  }

  io.data := table(io.address)
}
```



# Summary

- ▶ External inputs need processing
- ▶ Minimum is a input synchronizer
- ▶ Communicating circuits/FSMs need handshaking
- ▶ Ready-valid interface
- ▶ Scala can be used to write circuit *generators*
- ▶ We explored generation of a binary to BCD conversion table